



For Semester II  
Basic Electronics Lab (301)

For CT only

Practical

**301**

Department of Electrical and Electronics Engineering

**MEASUREMENT OF RESISTANCE OF CARBON RESISTORS**

**AIM**

- To identify resistor values and tolerances from the color code and multimeter measurement.
- To compare the color coded resistor value with the actual measured resistance value (by multimeter or ohmmeter).

**COMPONENTS REQUIRED**

Sl no	Components	Specification	Quantity
1	Resistor	-	Any five with different value
2	Multimeter	0-100kΩ	1 No.

**THEORY**

Since it is not practical to print the resistance values on the resistors due to its small size, therefore a method called color coding is adopted.


The resistor values are generally printed on the body of bigger resistors like wire wound and metal film type resistors, but for the carbon resistors the values are color coded since its size is too small to print the value directly on the body of resistor. Colour coding is standardized by Electronic Industries Association(EIA). Coloured bands are marked on the surface of the resistors from one end. The 1<sup>st</sup> band gives the first significant digit, 2<sup>nd</sup> band gives second significant digit of the resistance value, 3<sup>rd</sup> band is the multiplier and 4<sup>th</sup> band represents the tolerance in percentage.

**PROCEDURE**

- Hold the resistor so that the colour band are at the left end of the resistor . write down the numerical value of first colour band
- Write down the numerical value of the second colour band at the right side of first numeric
- Read the numerical value of third colour band and write down those many zeros at the right side of the first two numeric
- Write down the tolerance in percentage on right side of above numerical values
- Measure the actual resistance using multimeter or ohm meter. Compare the colour code value with multimeter reading.
- Repeat the procedure for various resistors

**TABULATION**

Sl No	First digit	Second digit	Third digit	Tolerance	Resistance value	Multimeter reading

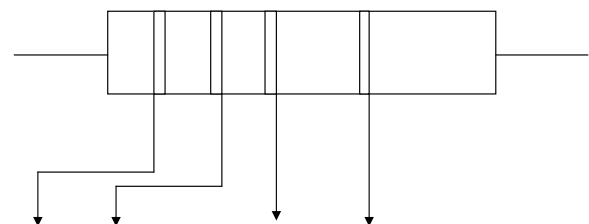

Color	1 <sup>st</sup> band	2 <sup>nd</sup> band	3 <sup>rd</sup> band (multiplier)	4 <sup>th</sup> band (tolerance)	Temp. Coefficient
Black	0	0	$\times 10^0$		
Brown	1	1	$\times 10^1$	$\pm 1\%$ (F)	100 ppm
Red	2	2	$\times 10^2$	$\pm 2\%$ (G)	50 ppm
Orange	3	3	$\times 10^3$		15 ppm
Yellow	4	4	$\times 10^4$		25 ppm
Green	5	5	$\times 10^5$	$\pm 0.5\%$ (D)	
Blue	6	6	$\times 10^6$	$\pm 0.25\%$ (C)	
Violet	7	7	$\times 10^7$	$\pm 0.1\%$ (B)	
Gray	8	8	$\times 10^8$	$\pm 0.05\%$ (A)	
White	9	9	$\times 10^9$		
Gold			$\times 10^{-1}$	$\pm 5\%$ (J)	
Silver			$\times 10^{-2}$	$\pm 10\%$ (K)	
None				$\pm 20\%$ (M)	

**RESULT**

Measured the resistance value using colour code and compared it with multimeter reading.

## CHARACTERISTICS OF P-N JUNCTION DIODE

### AIM

To determine the forward characteristics of a p-n junction diode and determine the static and dynamic resistance.

### COMPONENTS AND EQUIPMENTS REQUIRED

SI No	NAME	SPECIFICATION	QUANTITY
1	POWER SUPPLY	0-30V	1 NO
2	VOLTMETER	0-20V	1 NO
3	AMMETER	0-100 $\mu$ A	1 NO
4	ZENER DIODE	5.6 V	1 NO
5	RESISTOR	1K $\Omega$	1 NO
6	POTENTIOMETER	1K $\Omega$	1 NO
7	BREAD BOARD		1NO
8	CONNECTING WIRES		AS REQUIRED

### THEORY

When a P type and N type semiconductors are joined together, a junction diode is created. It has a unique ability to permit current only in one direction. The lead connected to P type is called anode and the lead connected to N type is called cathode. If the anode of the diode is connected to the +ve terminal of a battery and cathode to the -ve terminal, the set up is called forward bias. The diode does not pass any current till the battery voltage exceeds the potential barrier (


0.7 V for Si & 0.3 V for Ge). Once the battery potential exceeds the barrier potential high forward current in the order of mA flows through the diode due to the movements of hole and electrons.

The static resistance or DC resistance is the ratio of DC voltage across the diode to the DC current flows through it. Dynamic resistance or AC resistance of the diode at any point is the reciprocal of the slope of the characteristic at that point.

ie dynamic resistance = change in voltage / change in current =  $\Delta V / \Delta I$
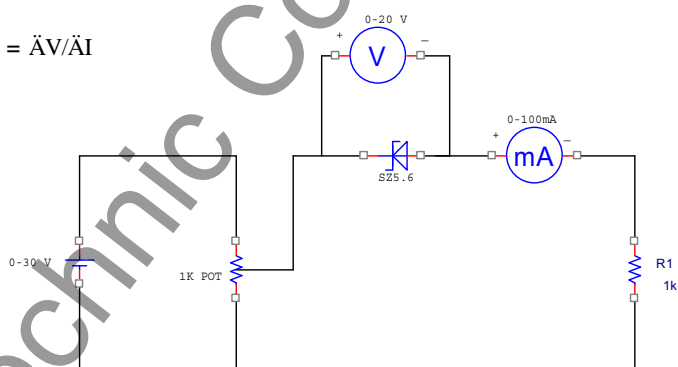
### PROCEDURE

- Set up the circuits as shown in figure on bread board.
- Switch on the power supply
- Varying the voltage across the diode in steps and find corresponding current.
- Repeat the above steps for different values of voltage



### TABULATION

V in volt	I in mA

### RESULT

Plotted the forward characteristics of PN junction Si diode and its

Static resistance = .....

Dynamic resistance = .....

## V-I CHARACTERISTICS OF ZENER DIODE

### AIM

To plot VI characteristics of a zener diode and determine the breakdown voltage ( $V_{BR}$ ) and dynamic resistance.

### COMPONENTS AND EQUIPMENTS REQUIRED

SI No	NAME	SPECIFICATION	QUANTITY
1	POWER SUPPLY	0-30V	1 NO
2	VOLTMETER	0-20V	1 NO
3	AMMETER	0-100 $\mu$ A	1 NO
4	ZENER DIODE	5.6 V	1 NO
5	RESISTOR	1K $\Omega$	1 NO
6	POTENTIOMETER	1K $\Omega$	1 NO
7	BREAD BOARD		1NO
8	CONNECTING WIRES		AS REQUIRED


### THEORY

An ordinary diode will not permit current when it is reverse biased. If the reverse biased voltage exceed the peak inverse voltage rating diode may get destroyed, due to avalanche break down. Zener diodes are special kind of diode designed to operate in the break down region without causing the damage to them. When diode is heavily doped its depletion layer become very narrow. When the applied reverse bias voltage across the diode is increased, the electric field across the depletion layer becomes more intense and electrons get pulled out from the

covalent bond, generating electron-hole pairs. Thus heavy reverse current flows. This phenomenon is called zener breakdown.
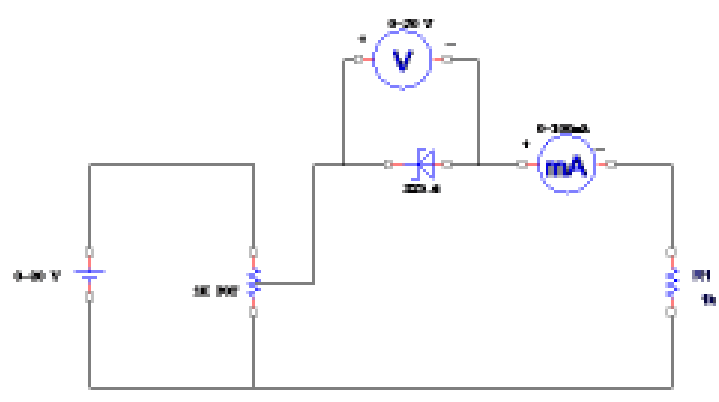
### PROCEDURE

- Wire the circuit as shown in fig. after testing the component.
- Vary the input voltage and note down the ammeter and voltmeter readings and enter it in the tabular column.
- Calculate the dynamic zener resistance.



**TABULATION**

V in volt	I in mA

**RESULT**

Plotted the VI characteristics of Zener diode and its  
 Break down voltage ( $V_{BR}$ ) = .....  
 Dynamic resistance = .....

**HALFWAVE RECTIFIER**

**AIM**

To study the characteristics of a half wave rectifier.

**COMPONENTS AND EQUIPMENTS REQUIRED**


SI No	NAME	SPECIFICATION	QUANTITY
1	TRANSFORMER	0-12V	1 NO
2	DIODE	1N 4001	1 NO
3	RESISTOR	1K $\Omega$	1 NO
4	CAPACITOR	470 $\mu$ F , 25 V	1 NO
5	BREAD BOARD		1 NO
6	CONNECTING WIRES		AS REQUIRED

**THEORY**

A rectifier converts AC to pulsating DC by eliminating the negative half cycle of the input voltage . During positive half cycle of the input voltage, upper end of the secondary of the transformer is positive and lower end is negative. Therefore the diode is forward biased and hence it conducts and out put voltage is equal to input voltage.

During negative half cycle of the input voltage, upper end of the secondary of the transformer is negative and lower end is positive. Therefore the diode is reverse biased and hence it does not conduct and out put voltage is equal to zero.  $V_{rms} = V_m / \sqrt{2}$   $V_{dc} = V_m / \pi$

Ripple factor= Ripple voltage/dc voltage

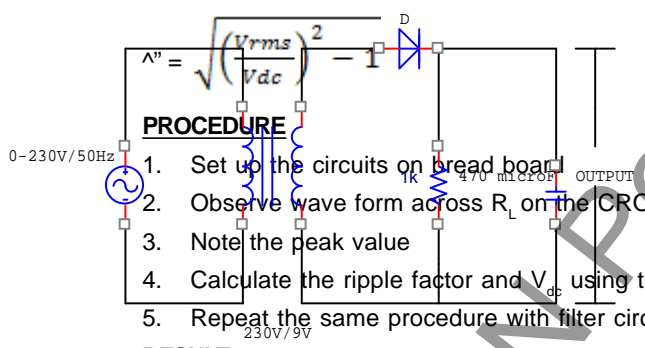

**PROCEDURE**

1. Set up the circuits on bread board.
2. Observe wave form across  $R_L$  on the CRO.
3. Note the peak value
4. Calculate the ripple factor and  $V_{dc}$  using the equations.
5. Repeat the same procedure with filter circuit.

**RESULT**

Studied the characteristics of half wave rectifier.  
 Theoretical value of ripple factor = .....  
 Practical value of ripple factor = .....  
 Difference between Theoretical value and Practical value = .....

**CENTRE TAPPED RECTIFIER**

**AIM**

To study the characteristics of a centre tapped rectifier.

**COMPONENTS AND EQUIPMENTS REQUIRED**

SI No	NAME	SPECIFICATION	QUANTITY
1	TRANSFORMER	9-0-9V	1 NO
2	DIODE	1N 4001	2 NO
3	RESISTOR	1K $\Omega$	1 NO
4	CAPACITOR	470 $\mu$ F , 25 V	1 NO
5	BREAD BOARD		1 NO
6	CONNECTING WIRES		AS REQUIRED

**THEORY**


A rectifier converts AC to pulsating DC. During positive half cycle of the input voltage, upper end of the secondary of the transformer is positive and lower end is negative. Therefore the diode  $D_1$  is forward biased and diode  $D_2$  is reverse biased .Therefore  $D_1$  conducts and out put voltage is equal to input voltage.

During negative half cycle of the input voltage, upper end of the secondary of the transformer is negative and lower end is positive. Therefore the diode  $D_1$  is reverse biased and diode  $D_2$  forward biased, hence it conducts and output voltage is same as that of positive half cycle.

$$V_{rms} = V_m / \sqrt{2} \quad V_{dc} = 2 V_m / \pi$$

Ripple factor = Ripple voltage/dc voltage
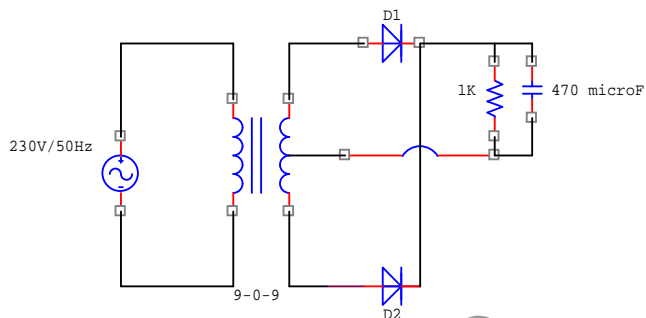
$$\Lambda'' = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$



### PROCEDURE

1. Set up the circuits on bread board
2. Observe the transformer secondary voltage( $V_{ac}$ ) and wave form across  $R_L$  on the CRO.
3. Note the peak value
4. Calculate the ripple factor and  $V_{dc}$  using the equations.
5. Repeat the same procedure with filter circuit.

### RESULT

Studied the characteristics of centre tapped rectifier.

Theoretical value of ripple factor =.....

Practical value of ripple factor =.....

## BRIDGE RECTIFIER

### AIM

To study the characteristics of a centre tapped rectifier.

### COMPONENTS AND EQUIPMENTS REQUIRED

Sl No	NAME	SPECIFICATION	QUANTITY
1	TRANSFORMER	0-12V	1 NO
2	DIODE	IN 4001	4 NO
3	RESISTOR	1KΩ	1 NO
4	CAPACITOR	470 μF , 25 V	1 NO
5	BREAD BOARD		1 NO
6	CONNECTING WIRES		AS REQUIRED

### THEORY

A rectifier converts AC to pulsating DC. During positive half cycle of the input voltage, upper end of the secondary of the transformer is positive and lower end is negative. Therefore the diode  $D_1$  and  $D_3$  are forward biased and diode  $D_2$  and  $D_4$  are reverse biased. Therefore diode  $D_1$  and  $D_3$  conducts and out put voltage is equal to the input voltage.

During negative half cycle of the input voltage, upper end of the secondary of the transformer is negative and lower end is positive. Therefore the diode  $D_1$  and  $D_3$  are reverse biased and diode  $D_2$  and  $D_4$  are forward biased, hence it conducts and out put voltage is same as that of positive half cycle.

$$V_{rms} = V_m / \sqrt{2} \quad V_{dc} = 2 V_m / \pi$$

Ripple factor= Ripple voltage/dc voltage

$$\Lambda'' = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

### PROCEDURE

1. Set up the circuits on bread board
2. Observe the transformer secondary voltage( $V_{ac}$ ) and wave form across  $R_L$  on the CRO.
3. Note the peak value
4. Calculate the ripple factor and  $V_{dc}$  using the equations.
5. Repeat the same procedure with filter circuit.

### RESULT

Studied the characteristics of bridge rectifier.

Theoretical value of ripple factor =.....

Practical value of ripple factor =.....

Difference between Theoretical value and Practical value =.....

**AIM**

To set up different clipping circuits using diode and observe the waveform.

**COMPONENTS AND EQUIPMENTS REQUIRED**

SI No	NAME	SPECIFICATION	QUANTITY
1	DIODE	IN 4001	1 NO
2	RESISTOR	3.3KΩ	1 NO
3	FUNCTION GENERATOR		1 NO
4	BREAD BOARD		1 NO
5	CONNECTING WIRES		AS REQUIRED

**THEORY**

The property of diode as a switching device is utilized in clipping circuit. They are useful to clip off positive or negative portion of the input waveform.

**POSITIVE CLIPPER**

This circuit passes only negative going half waves of the input to the output. All the positive half cycles are

bypassed through the diode since the diode gets forward biased when the input voltage becomes positive. Due to the voltage drop across the diode clipping occurs exactly at + 0.6V.

**NEGATIVE CLIPPER**

This circuit passes only positive going half waves of the input to the output. All the negative half cycles are bypassed through the diode since the diode gets forward biased when the input voltage becomes negative. Due to the voltage drop across the diode clipping occurs exactly at - 0.6V.

**PROCEDURE**

1. Set up the circuit and the signal generator in sine wave mode and fix the amplitude at 20 Vpp connecting directly with CRO
2. Connect the signal generator output to the input of the circuit.
3. Observe the clipped waveform on CRO screen

**RESULT**

Observed and plotted the clipped waveform.

**CLAMPING CIRCUITS**

To set up different clamping circuits using diode and observe the waveform.

**COMPONENTS AND EQUIPMENTS REQUIRED**

SI No	NAME	SPECIFICATION	QUANTITY
1	DIODE	IN 4001	1 NO
2	CAPACITOR	10μF	1 NO
3	FUNCTION GENERATOR		1 NO
4	BREAD BOARD		1 NO
5	CONNECTING WIRES		AS REQUIRED

**THEORY**

At some situations it is necessary to add or subtract a dc voltage to a given wave without changing the shape of waveform. Circuit used for this purpose is called clammer. The clamping level can be made at any voltage level by biasing the diode. Such a circuit is called biased clammer.

**Positive clammer**

During one negative half cycle of the input waveform the diode conducts and capacitor charges to  $V_m$  with positive polarity at right side of the capacitor. During positive half cycle of the input waveform, the capacitor cannot discharge since the diode does not conduct. Thus capacitor acts as a dc voltage source of  $V_m$  volts in series with the input signal voltage  $V_m$ . The output voltage then can be expressed as

$$V_o = V_m + V_m$$

**Negative clammer**

During one positive half cycle of the input waveform the diode conducts and capacitor charges to  $V_m$  with negative polarity at right side of the capacitor. During negative half cycle of the input waveform, the capacitor cannot discharge since the diode does not conduct. Thus capacitor acts as a dc voltage source of  $-V_m$  volts in series with the input signal voltage  $-V_m$ . The output voltage then can be expressed as

$$V_o = -V_m + -V_m$$

**PROCEDURE**

1. Set up the circuit and the signal generator in sine wave mode and fix the amplitude at 20 Vpp connecting directly with CRO
2. Connect the signal generator output to the input of the circuit.
3. Observe the clammer waveform on CRO screen

**RESULT**

Observed and plotted the clipped waveform

**VOLTAGE DOUBLER****AIM**

To set up study voltage doubler circuit.

**COMPONENTS AND EQUIPMENTS REQUIRED**

SI No	NAME	SPECIFICATION	QUANTITY
1	DIODES	IN 4001	2 NOS
2	CAPACITOR	100 $\mu$ F	2 NOS
3	VOLTMETER	0-30V	1 NO
4	FUNCTION GENERATOR		1 NO
5	BREAD BOARD		1 NO
6	CONNECTING WIRES		AS REQUIRED

**PROCEDURE**

1. After checking the components using multimeter, connections are made as per diagram.
2. Switch on the power supply.
3. Take the reading of input ac voltage, voltage across  $C_1$  and  $C_2$  and out put voltage.

**RESULT**

Studied and verified the voltage doubler circuit.

**THEORY**

The circuit of a voltage doubler is shown in figure. During the positive half cycle of the input voltage, the diode  $D_1$  conducts and  $D_2$  does not conduct and capacitor  $C_1$  charges to peak value  $V_m$ . During the negative half cycle of the input voltage the diode  $D_2$  conducts and  $D_1$  does not conduct and capacitor  $C_2$  charges to peak value  $V_m$ . Since capacitors  $C_1$  and  $C_2$  are in series out put voltmeter reads  $2V_m$ .

**COMMON EMITTER TRANSISTOR CHARACTERISTICS****AIM:**

To plot the VI characteristics of common emitter configuration of a given transistor and plot the DC load line.

**COMPONENTS AND EQUIPMENTS REQUIRED**

SI No	NAME	SPECIFICATION	QUANTITY
1	POWER SUPPLY	0-30 V	2 NOS
2	VOLTMETER	0-10V, 0-30V	1 EACH
3	AMMETER	0-100 mA, 0-100 $\mu$ A	1 EACH
4	TRANSISTOR	BC 107	1 NO
5	RESISTOR	1.5 K $\Omega$	1 NO
6	POTENTIOMETER	1 K $\Omega$	2 NOS
7	BREAD BOARD		1 NO
8	CONNECTING WIRES		AS REQUIRED

**THEORY**

A transistor is a 3 terminal active device. The 3 terminals are emitter(E),base(B)and collector(C).In CE configuration we make the emitter common to both input and output for normal operation.The base-emitter junction is forward biased and collector-emitter junction is reverse biased.

The input characteristics is plotted between input current( $I_B$ ) and the input voltage( $V_{BE}$ ) with keeping output voltage ( $V_{CE}$ ) constant. The input dynamic resistance  $r_i$  is calculated using the equation

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B}, \text{ keeping } V_{CE} \text{ is constant.}$$

The output characteristics is plotted between output current( $I_C$ ) and the output voltage( $V_{CE}$ ) with keeping input current ( $I_B$ ) constant.

The output dynamic resistance  $r_o$  is calculated using the equation

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}, \text{ keeping } I_B \text{ is constant.}$$

**PROCEDURE****For input characteristics**

1. Check the transistor using multimeter. Switch on the power supply keeping rheostat at minimum position. Switch off the collector to emitter power supply.
2. Note down the base current for different values of  $V_{BE}$ .
3. Repeat the step 2 for different values of  $V_{CE}$ , say 3V, 6V.
4. Draw the characteristics on a graph sheet and calculate dynamic input resistance.

**For out put characteristics**

1. Check the transistor using multimeter. Switch on the power supply keeping rheostat at minimum position. Switch off the base to emitter power supply.
2. Note down the collector current for different values of  $V_{CE}$ .
3. Repeat the step 2 for different values of base current, say 80 $\mu$ A, 100 $\mu$ A.
4. Draw the characteristics on a graph sheet and calculate dynamic out put resistance.

**TABULATION****Input characteristics**

$V_{CE} = 0V$		$V_{CE} = 3V$		$V_{CE} = 6V$	
$I_B$	$V_{BE}$	$I_B$	$V_{BE}$	$I_B$	$V_{BE}$

**Out put characteristics**

$I_B = 60\mu A$		$I_B = 80\mu A$		$I_B = 100\mu A$	
$I_C$	$V_{CE}$	$I_C$	$V_{CE}$	$I_C$	$V_{CE}$

**RESULT**

Plotted the input and out put characteristics of a CE transistor.

Dynamic input resistance = .....

Dynamic out put resistance = .....