

TED (10)-3004  
(REVISION-2010)

Reg. No. ....  
Signature .....

SECOND SEMESTER DIPLOMA EXAMINATION IN ELECTRICAL AND  
ELECTRONICS ENGINEERING—MARCH, 2013

**BASIC ELECTRICAL ENGINEERING**

[Time : 3 hours

(Maximum marks : 100)

PART—A

Marks

I Answer all questions in one or two sentences. Each question carries 2 marks.

1. Define specific resistance of materials.
2. Define Kirchoff's voltage law.
3. Define the term break down voltage.
4. What is flux density ?
5.  $A = 20 \angle 60^\circ$ ,  $B = 5 \angle 30^\circ$ . Find  $A \times B$  and  $A/B$ .

(5×2=10)

PART—B

II Answer any five of the following questions. Each question carries 6 marks.

1. State Superposition theorem.
2. Draw the B-H curve and explain the various regions of the curve.
3. Define :
  - (i) RMS value
  - (ii) Average value
  - (iii) Instantaneous value of an alternating quantity.
4. What is resonance in RLC series circuits ? Derive the equation for resonance frequency.
5. Define :
  - (i) Admittances
  - (ii) Susceptences
  - (iii) Conductances.
6. Derive an expression for the magnetising force of a long straight current carrying conductor.
7. Differentiate statically and dynamically induced emf.

(5×6=30)

## PART—C


(Answer one full question from each unit. Each question carries 15 marks.)

## UNIT—I

- III (a) State Thevenin's theorem. 6
- (b) A coil of relay made of copper wire. At a temperature of  $20^{\circ}\text{C}$ , the resistance of the coil is  $400\Omega$ . Calculate the resistance of the coil at temperature of  $80^{\circ}\text{C}$ . The temperature coefficient of copper is  $0.0038\Omega/\Omega/^{\circ}\text{C}$  at  $0^{\circ}\text{C}$ . 9

OR

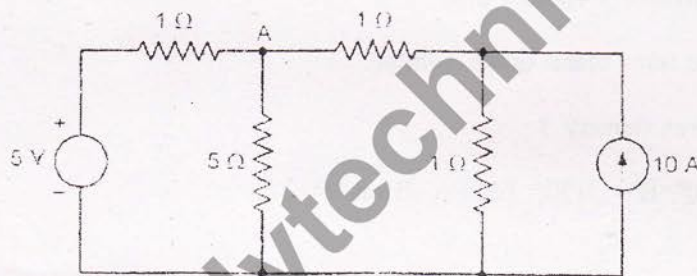- IV (a) State maximum power transfer theorem. 6
- (b) Find, using Thevenin's theorem, the current in the  $5\Omega$  resistor connected across AB in the network shown in figure. 9



## UNIT—II

- V (a) Compare magnetic circuit and electric circuit with respect to their similarities. 6
- (b) Two capacitors have capacitances of  $6\mu\text{F}$  and  $10\mu\text{F}$  respectively :
- (i) Find the total capacitance when they are connected (a) in parallel (b) in series.
- (ii) When the above two capacitance are connected in series across a  $200\text{V}$  supply, find the potential difference across each capacitor and the charge on each capacitor. 9

OR

- VI (a) Derive the expression for capacitance of an isolated sphere. 6
- (b) A rectangular shaped core is made of mild steel plate  $15\text{mm} \times 20\text{mm}$  cross section.. The mean length of magnetic path is  $18\text{cm}$ . The exciting coil has 300 turns and current  $0.7\text{A}$ . Calculate:
- (i) Magnetising force
- (ii) Flux density
- (iii) Reluctance
- (iv) Flux of magnetic circuit. Assume relative permeability of mild steel as 940. 9



## UNIT—III

- VII (a) Define self inductance and mutual inductance. 8
- (b) Two coils have a mutual inductance of 0.3H. If the current in one coil is varied from 5A to 2A in 0.4S, calculate the average emf induced in the second coil. 7

OR

- VIII (a) Describe the phase and phase difference of alternating voltage and current. 6
- (b) An alternating voltage as given by  $V = 141.4 \sin 314t$ . Find :
- (i) frequency (iii) average value
- (ii) rms value (iv) the instantaneous value of voltage when  $t$  is 3ms. 9

## UNIT—IV

- IX (a) Explain RLC series circuit with wave form and phasor diagram. 6
- (b) A non inductive resistance of  $10\Omega$  is connected in series with an inductive coil across 20V, 50Hz. AC supply. The current drawn by the series combination is 10A. The resistance of the coil is  $2\Omega$ . Determine :
- (i) Inductance of the coil (ii) Power factor of the circuit. 9

OR

- X (a) Explain impedance and impedance triangle. 6
- (b) The following diagram shows a parallel R-L arrangement connected across 200V, 50Hz AC supply. Calculate :
- (i) the current drawn from the supply (iii) real power
- (ii) apparent power (iv) reactive power.

