

THIRD SEMESTER DIPLOMA EXAMINATION IN ENGINEERING/
TECHNOLOGY—MARCH, 2014

ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to AU, ME and TD)

[Time : 3 hours

(Maximum marks : 100)

PART—A

(Maximum marks : 10)

Marks

I Answer all questions in one or two sentences. Each question carries 2 marks.

1. Define Ampere hour rating of a lead acid battery.
2. Write the equation for power in three phase ac star connected circuit.
3. Draw a three phase delta connection.
4. List any two applications of three phase squirrel cage induction motor.
5. Draw a bridge rectifier circuit.

(5×2=10)

PART—B

(Maximum marks : 30)

II Answer *any five* of the following questions. Each question carries 6 marks.

1. Explain construction of positive plate of the 24V, lead acid battery with a neat sketch.
2. Describe the chemical reactions in a 12V lead acid cell during charging and discharging.
3. Explain working of a single phase, core type, 230/110V, 3kVA, two winding transformer with a neat sketch.
4. Draw internal wiring diagram of a direct on line starter.
5. Explain the construction of a three phase squirrel cage induction motor.
6. Discuss the biasing of a PNP transistor in Common Base active region with the sketch.
7. Draw truth tables of :

(i) NOR gate

(iii) NAND gate

(ii) Ex-OR gate

(5×6=30)

PART—C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each question carries 15 marks.)

UNIT—I

- III (a) Write any two safety precautions to be observed while working with Lead acid battery. 2
- (b) Explain construction of a DC shunt generator. 6
- (c) Discuss any two methods of charging Lead acid battery. 7

OR

- IV (a) State working principle of a dc motor. 2
- (b) Describe care and maintenance activities for a lead acid Battery. 6
- (c) Justify the usage of a three point starter with a DC Shunt motor by clearly stating the functions of starting resistors, no volt coil and over load trip. 7

UNIT—II

- V (a) Draw three phase Star connection. 2
- (b) Explain working of a single phase welding transformer with a schematic diagram. 6
- (c) Compute the value of current I in a RLC ac circuit in which a $2\ \Omega$ resistor, a 0.05 henry inductance and a 100 micro farad capacitance are connected in series and fed with a supply of 100V at 50Hz. 7

OR

- VI (a) Specify the relation between phase and line values of voltage and current in a three phase delta connection. 2
- (b) Explain working of an auto transformer with a neat diagram. 6
- (c) Compute the active power input to a delta connected three phase induction motor which takes a phase current of 5A when a line voltage of 415 V is applied. Power factor of the motor is 0.7. 7

UNIT—III

- VII (a) State the basic principle of induction heating. 2
- (b) Explain the construction of an Arc furnace. 6
- (c) Demonstrate the working of a single phase, capacitor start induction motor with a neat diagram. 7

OR


- VIII (a) Specify any two industrial applications of electric heating. 2
- (b) Differentiate Induction heating and Dielectric heating. 6
- (c) Explain working of a Moving coil ammeter with a neat sketch. 7

UNIT—IV

- IX (a) Write any two industrial applications of an SCR. 2
- (b) Describe a RC coupled Common Emitter amplifier with diagram. 6
- (c) Demonstrate the working of an NPN transistor in the active region with a neat schematic Diagram. 7

OR

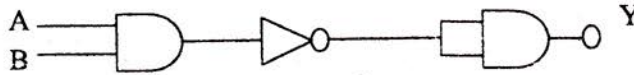- X (a) List any two configurations of transistors. 2
- (b) Draw the truth table of the following logic circuit. 6



- (c) Explain rectifier action of a centre tapped full wave rectifier with a neat circuit diagram. 7