

TED (10)–3053

(REVISION—2010)

Reg. No.

Signature

THIRD SEMESTER DIPLOMA EXAMINATION IN ELECTRICAL AND
ELECTRONICS ENGINEERING—MARCH, 2013

ELECTRONIC DEVICES AND CIRCUITS

[Time : 3 hours

(Maximum marks : 100)

Marks

PART—A

(Maximum marks : 10)

I Answer *all* questions in one or two sentences. Each question carries 2 marks.

1. What is meant by diffusion current ?
2. List out any two applications of a diode.
3. Define the peak inverse voltage.
4. Define faithful amplification.
5. State two conditions for the sustained oscillation.

(5x2=10)

PART—B

(Maximum marks : 30)

II Answer *any five* questions. Each question carries 6 marks.

1. Compare the ordinary diode with zener diode.
2. Analyse the working of a diode as a rectifier.
3. Illustrate the wave forms of a full wave rectifier with a capacitor filter.
4. Draw the circuit diagram of a bridge rectifier.
5. Write any three applications of Schmitt trigger circuit.
6. List out the various types of couplings of amplifiers.
7. Differentiate class A and class B amplifiers.

(5x6=30)

PART—C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each question carries 15 marks.)

UNIT – I

- III (a) Illustrate the reverse characteristic of a zener diode. 8
(b) Explain the working of a transistor as an amplifier. 7

OR

- | | | |
|--------|--|---|
| IV (a) | Establish the relation between the β and α in a transistor. | 7 |
| (b) | Draw the common emitter amplifier circuit using a transistor and explain the phase reversal in the output. | 8 |

UNIT - II

- | | | |
|-------|---|---|
| V (a) | Compare half wave and full wave rectifiers. | 8 |
| (b) | Explain the working of a regulator using 7805 IC. | 7 |

OR

- | | | |
|--------|---|---|
| VI (a) | What is a clipping circuit ? Explain the working of a positive shunt clipper using diode. | 8 |
| (b) | Explain the working of a capacitor filter in a rectifier circuit. | 7 |

UNIT - III

- | | | |
|---------|--|---|
| VII (a) | Draw the circuit of a push pull amplifier and explain its working. | 8 |
| (b) | Explain the operation of a single stage power amplifier. | 7 |

OR

- | | | |
|----------|--|---|
| VIII (a) | Explain the working of a complementary-symmetry push pull amplifier with a neat circuit diagram. | 8 |
| (b) | Draw the frequency response of a RC coupled amplifier and mark various points on it. | 7 |

UNIT - IV

- | | | |
|--------|--|---|
| IX (a) | With the help of a circuit diagram, explain the working of a Hartley oscillator. | 8 |
| (b) | Describe the working of an astable multivibrator circuit using transistors. | 7 |

OR

- | | | |
|-------|--|---|
| X (a) | Describe the operation of a RC phase shift oscillator with a neat circuit diagram. | 8 |
| (b) | Develop an astable multivibrator circuit using 555 timer IC. | 7 |